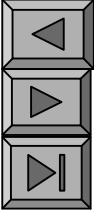



↖ Bode



11-1


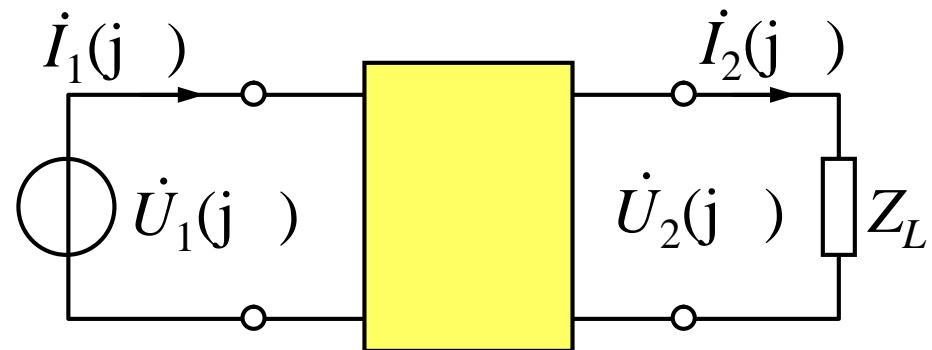
$$H(j\omega) = \frac{\dot{R}_k(j\omega)}{\dot{E}_{sj}(j\omega)}$$





$$H(j\omega) = \frac{\dot{U}_2(j\omega)}{\dot{U}_1(j\omega)}$$

$$H(j\omega) = \frac{\dot{U}_2(j\omega)}{\dot{I}_1(j\omega)}$$

$$H(j\omega) = \frac{\dot{I}_2(j\omega)}{\dot{U}_1(j\omega)}$$
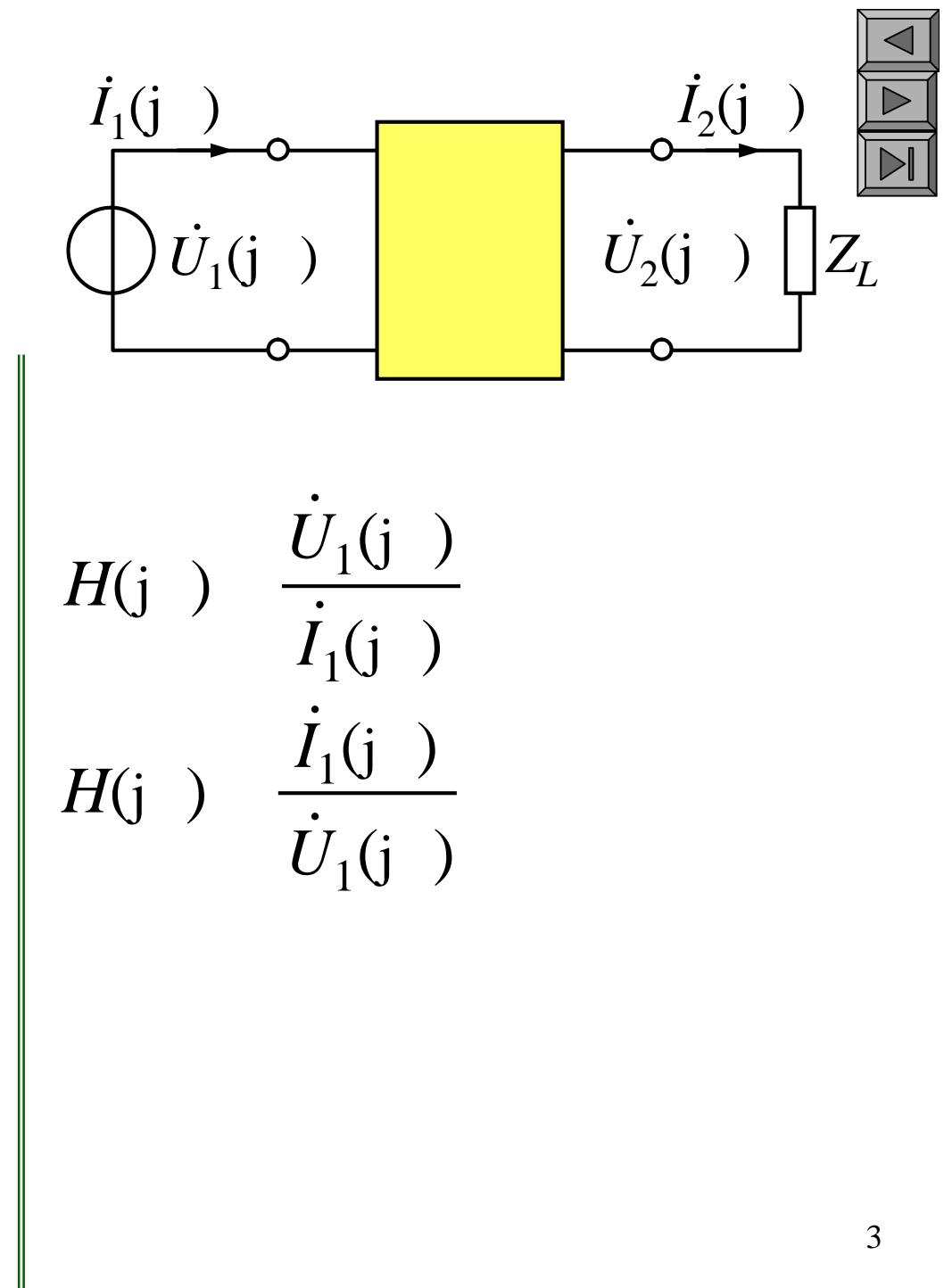
$$H(j\omega) = \frac{\dot{I}_2(j\omega)}{\dot{I}_1(j\omega)}$$



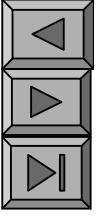

11-1 RLC



RLC

u

i

$C \quad L$

f

()

1.

$$\begin{array}{ccc} Z & R & j(X_L \ X_C) \\ X_L & X_C & 0 \\ Z & R \end{array}$$




$$L \quad \frac{1}{C}$$



$$\frac{1}{\sqrt{LC}}$$


$$f \quad \frac{1}{2 \sqrt{LC}}$$

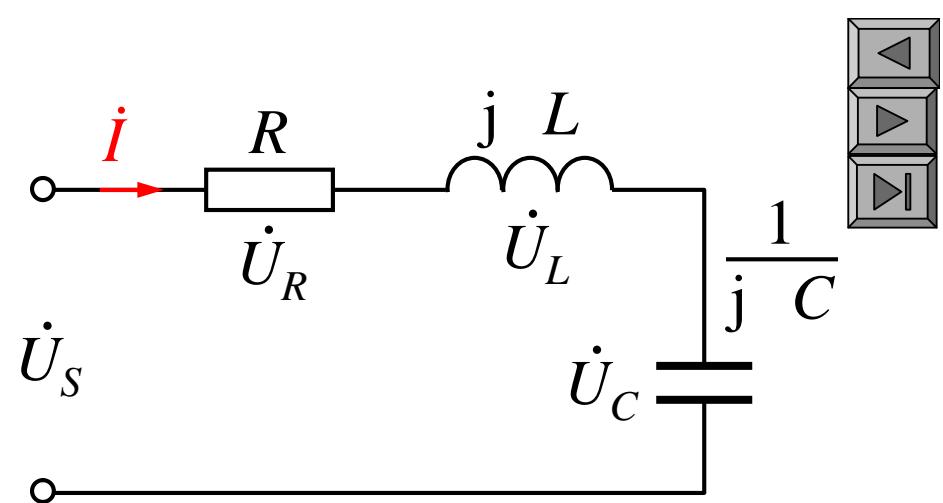

RLC

L C

R

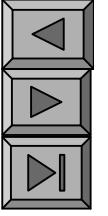

(1) $L \quad C$

(2) f


2.

(1)


(2) $Z(j\omega) = R$

$f \quad L \quad C$

$L \quad C \quad C$

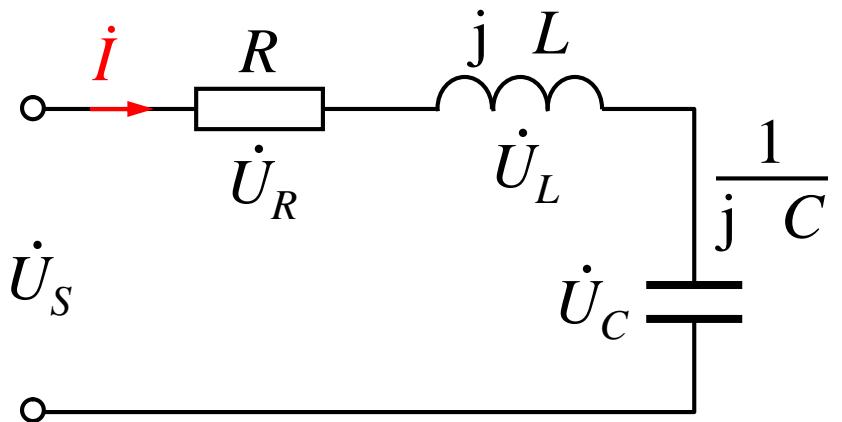


$$|I(j\omega)| = \frac{|U_s(j\omega)|}{R}$$

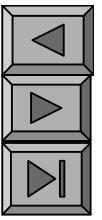

$|Z(j_-)|$

$Z(j_-) \approx R+j_-L$

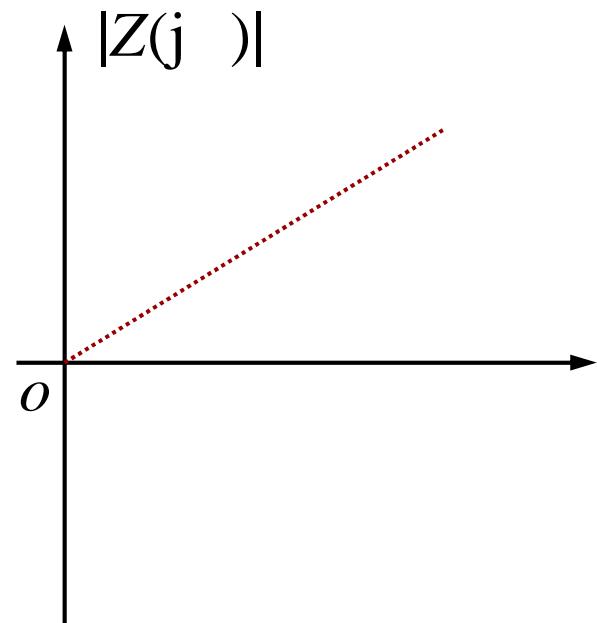

(3)

$$U_X(j_0) \quad 0 \\ U_C(j_0)$$



$$U_L(j_0)$$

$$U_L(j_0) = 0L I(j_0) = 0L \frac{U_S}{R} = Q U_S$$

$$U_C(j_0) = \frac{1}{0C} I(j_0) = \frac{1}{0C} \frac{U_S}{R} = Q U_S$$


$$Q = \frac{0L}{R} = \frac{1}{0CR} = \frac{1}{R} \sqrt{\frac{L}{C}}$$
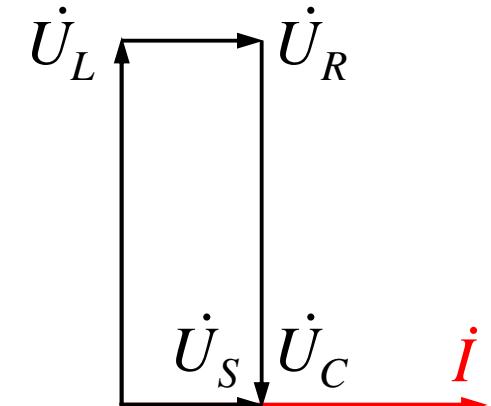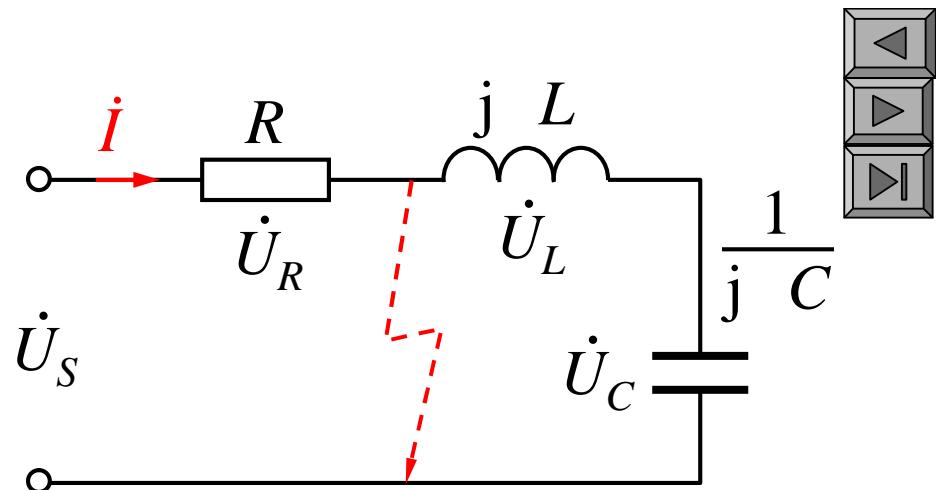
$$\frac{U_L(j_0)}{U_S} = \frac{U_C(j_0)}{U_S}$$



$$0L \quad \frac{1}{0C} \quad R \quad Q$$

$$U_L(j_0) \quad U_C(j_0) \quad U_S$$

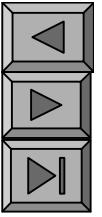

L C



L C

$$L \ 0.3\text{mH} \quad R \ 10 \text{ } 560\text{kHz}$$

$$1.5 \text{ V}$$


$$C \quad \frac{1}{(2 \pi f_0)^2 L} \quad 269\text{pF}$$

$$I_0 \quad \frac{U}{R} \quad \frac{1.5}{10} \text{ A}$$


$$U_C \quad I_0 \frac{1}{\sqrt{LC}} \text{ V} \quad 1.5 \text{ V}$$

$$Q \quad 106$$

C

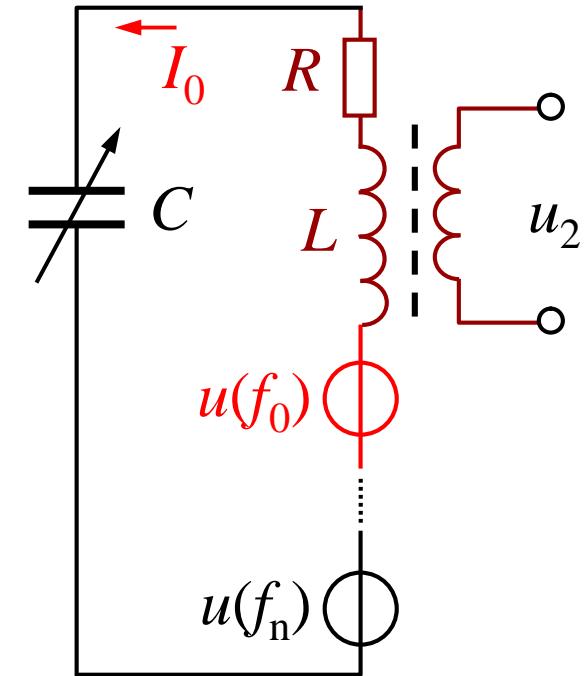

$$\frac{Q}{L}$$

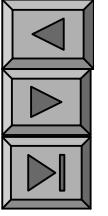



(4)

$$P(j_0) = U_S I(j_0) = I^2(j_0)R$$

$$Q(j_0) = Q_L(j_0) = Q_C(j_0)$$
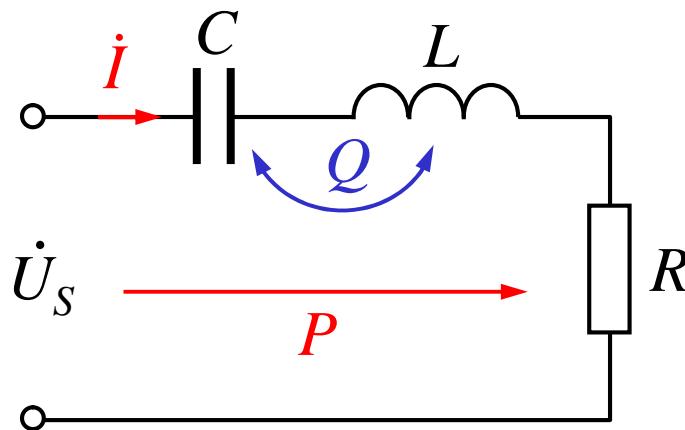
$$I_0 L^2(j_0) = \frac{1}{C_0} I^2(j_0)$$



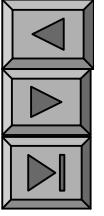

(5)

$$i = I_m \cos \omega t$$

$$u_C = U_{Cm} \sin \omega t + I_m L_0 \sin \omega t$$

$$w_L = \frac{1}{2} L i^2 = \frac{1}{2} L I^2 \cos^2 \omega t$$

$$w_C = \frac{1}{2} C u_C^2 = \frac{1}{2} C U_C^2 \sin^2 \omega t$$



$$W =$$

$$W_L =$$


$$W_C =$$

$$LI^2$$

$$CU_C^2$$

$$CQ^2U_S^2$$



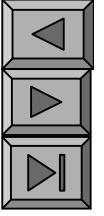

$$Q = \frac{\frac{0L}{R} - \frac{0}{R} \frac{L I^2(j_0)}{I^2(j_0)}}{\frac{|Q_L(j_0)|}{P(j_0)} + \frac{|Q_C(j_0)|}{P(j_0)}}$$

$$\frac{L I^2(j_0)}{T_0 R I^2(j_0)} \rightarrow$$


!

Q

Q

“ ”

Q

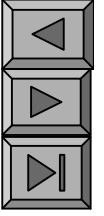


11-3 RLC



$L \quad C$

u_S


R

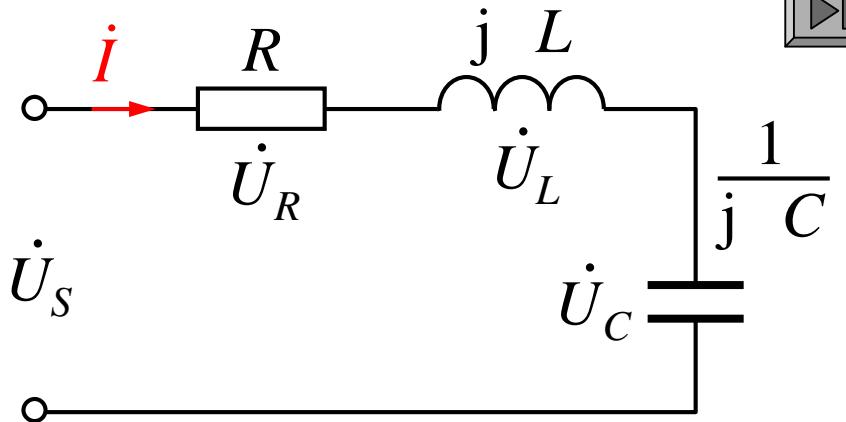


—
0

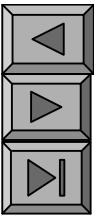1.

$$H_R(j\omega) = \frac{\dot{U}_R(j\omega)}{\dot{U}_S(j\omega)} = \frac{R}{Z(j\omega)}$$



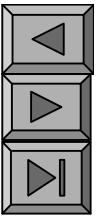


0

0

1

2

0

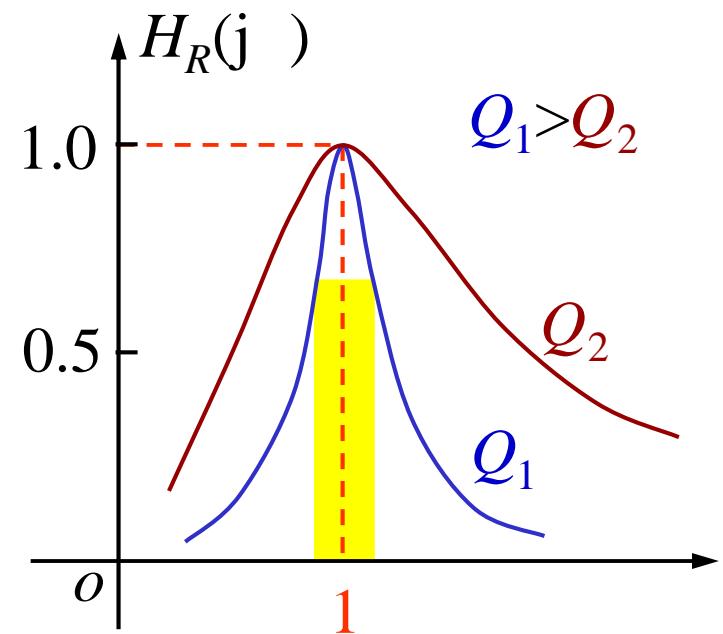


蠟

0

蠟 Q

0

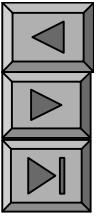

!

()

0.707

j2 j1)


j1

j2

$$\frac{1}{\sqrt{1 - Q^2 - \frac{1}{j^2})^2}} \quad \frac{1}{\sqrt{2}}$$

$$Q^2 - \frac{1}{j^2} - 1$$


2010 3 3

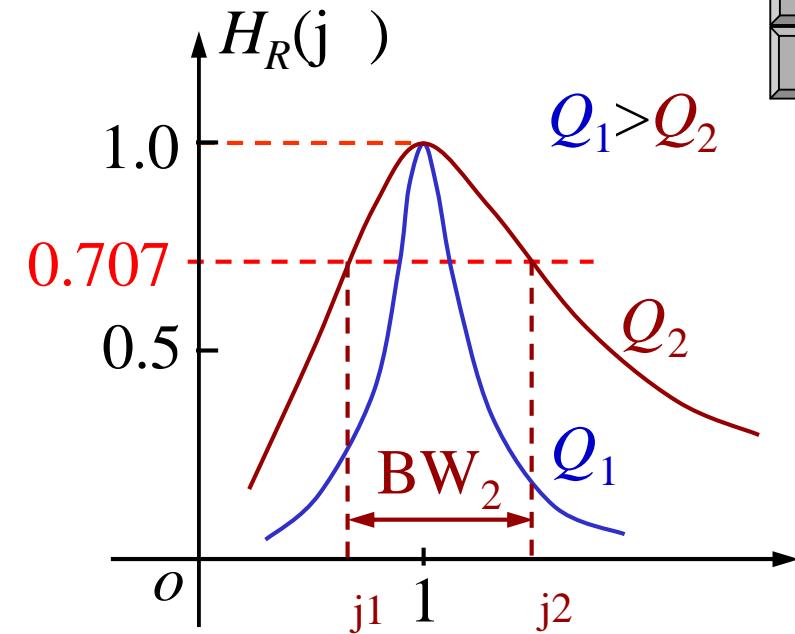

$$Q - \frac{1}{j^2} - 1$$

$$BW - \frac{j^2}{j^2 - j^1} - \frac{1}{Q}$$
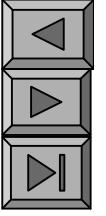
$$BW - \frac{j^2}{j^2 - j^1} - \frac{0}{Q}$$





$$BW \quad j_2 \quad j_1 \quad \frac{0}{Q} \quad Q$$



Q


BW

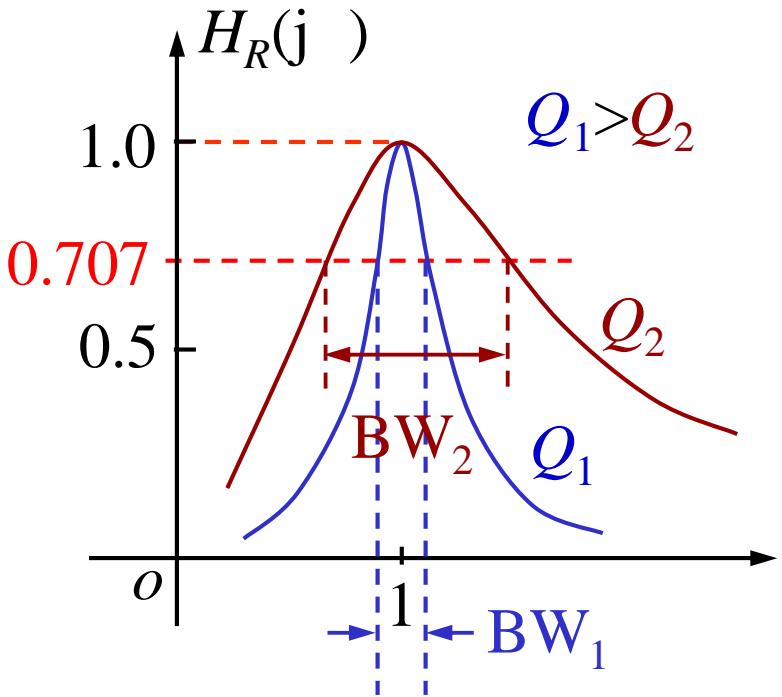


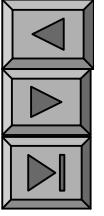

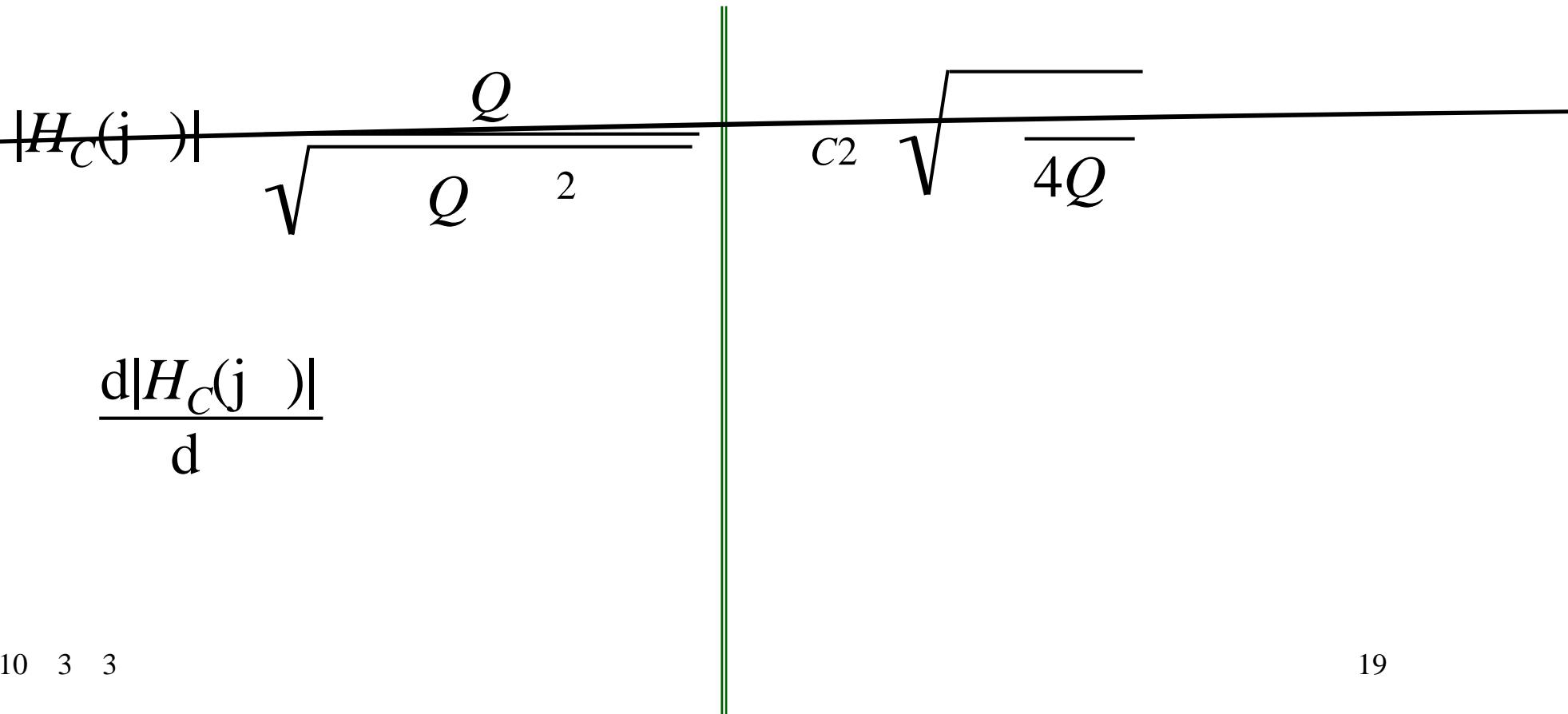2.

$$H_C(j\omega) = \frac{\dot{U}_C(j\omega)}{\dot{U}_S(j\omega)} = \frac{jQ}{jQ^2} = \frac{1}{jQ}$$
$$\dot{U}_C(j\omega) = \dot{U}_R(j\omega) 90^\circ$$



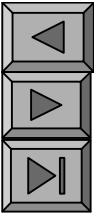


$$c_2 \sqrt{\frac{Q}{4Q}} = 1$$


$$|H_C(j\omega)| = \frac{Q}{\sqrt{\frac{Q}{4Q}}} = Q$$

$$Q = \frac{1}{\sqrt{2}}$$

$$Q \quad c_2 \quad 1$$

$$|H_C(j\omega)| \quad 1 \quad Q$$

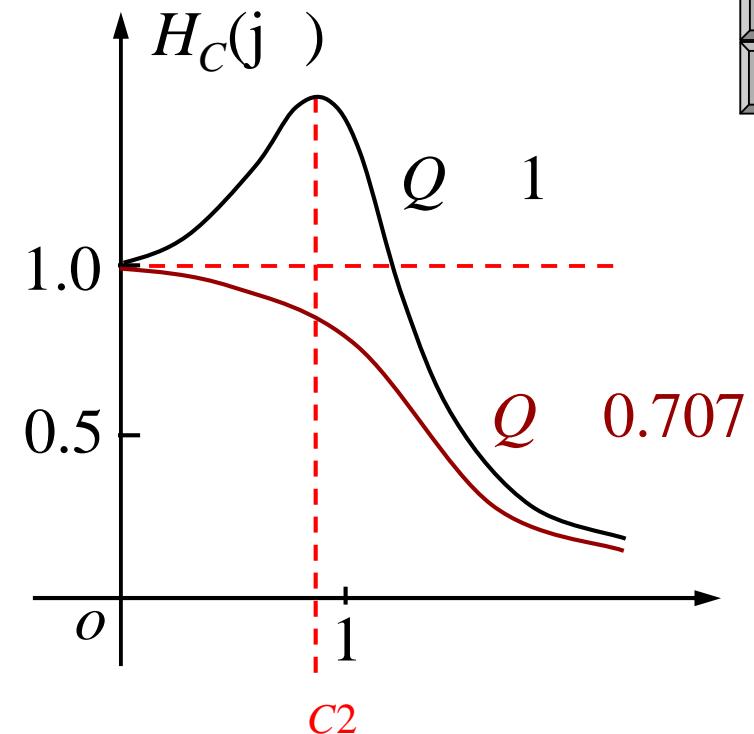


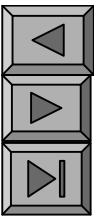



$$|H_C(j\omega)| = \frac{1}{\sqrt{2}}$$

$$j = 1.55 \quad 0 \\ 0 \sim j$$


3.

$$|H_L(j\omega)| = |H_C(j\omega)|$$

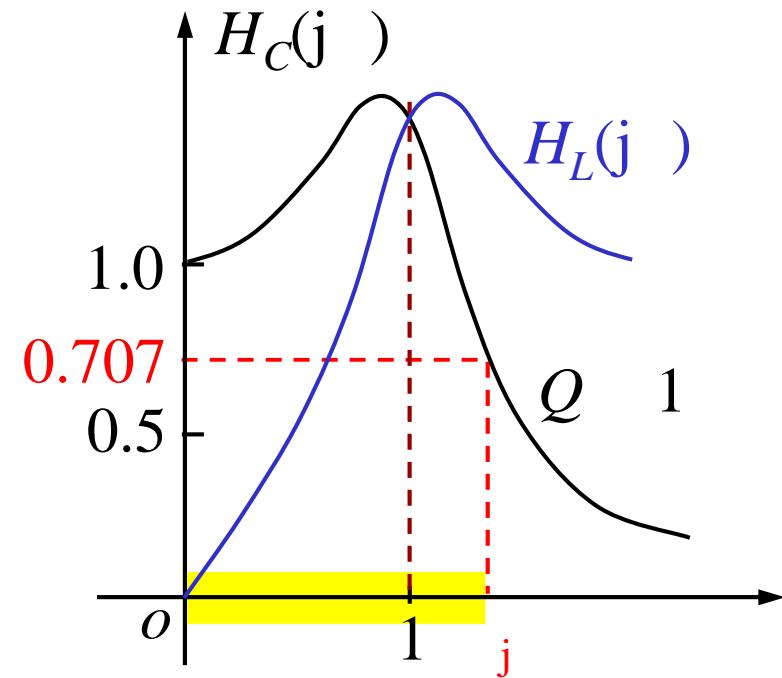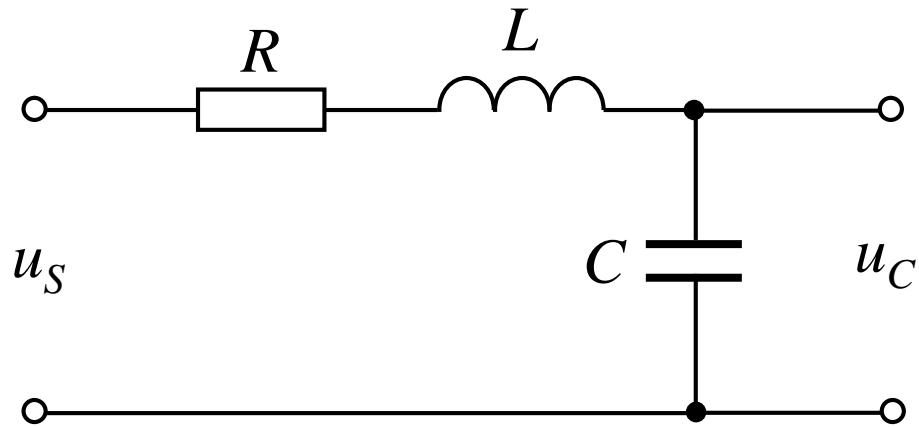

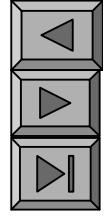

11-4 RLC

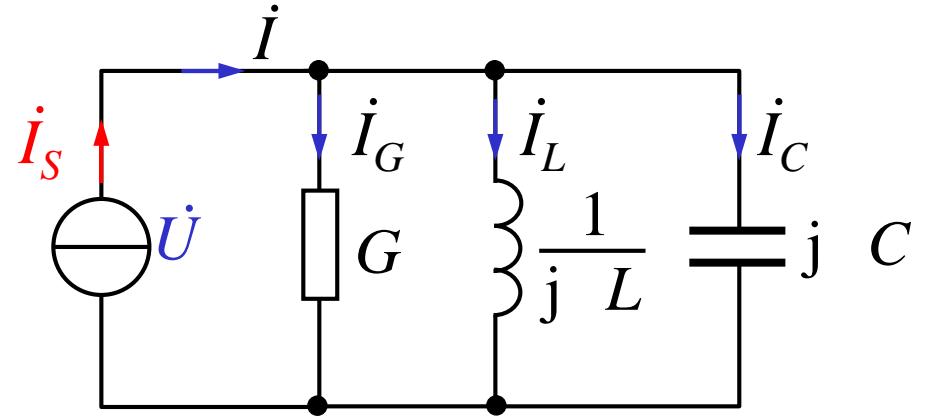

$$Y(j\omega) = G + j(C - \frac{1}{j\omega L})$$

1.

$$\frac{1}{j\omega C} = \frac{1}{j\omega_0 C} = \frac{1}{\sqrt{LC}}$$



$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$



$$f_0$$


$$G = \frac{L}{C}$$

2.


(1)

(2)

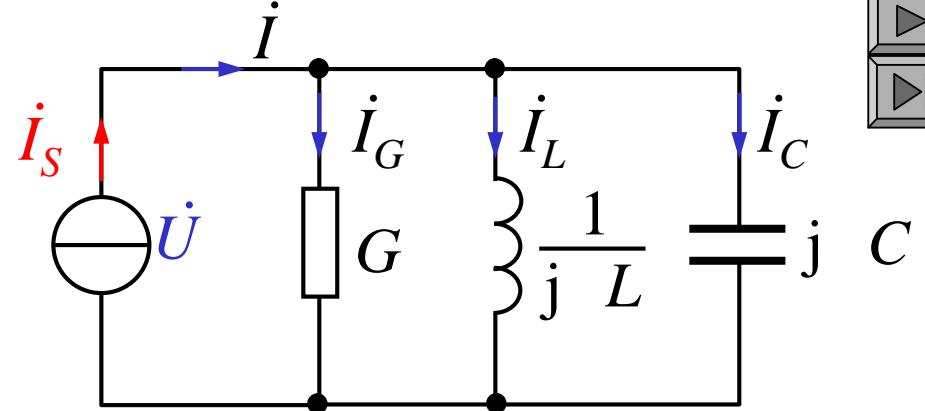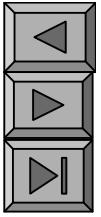

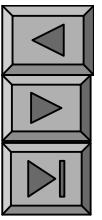

$$I_L(\cdot_0)$$


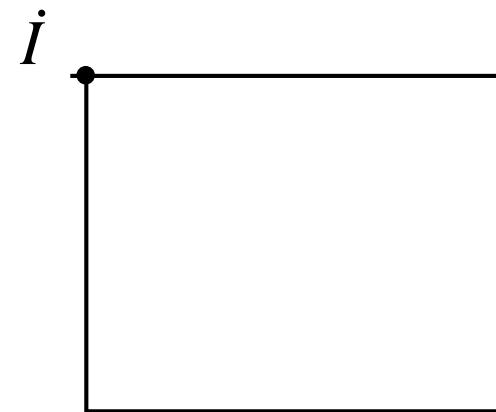


3.

$$Q_C = \frac{1}{0} C U^2$$

$$Q_L = \frac{1}{0} L U^2$$

\mathcal{Q}

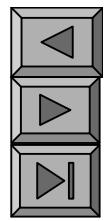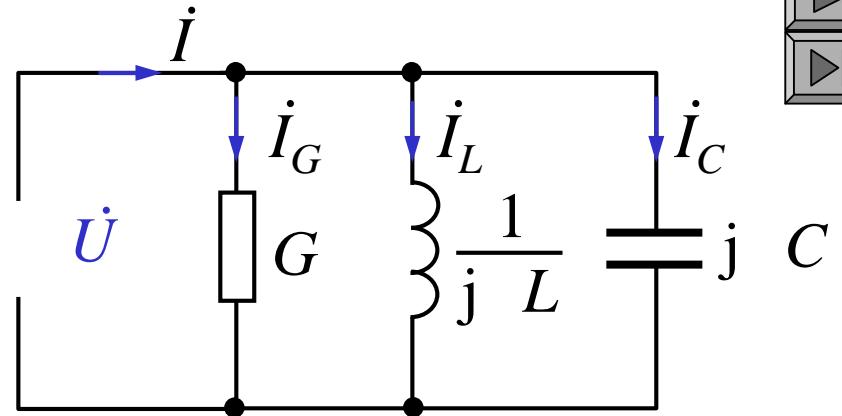

4.

$$Y(j\omega) = j\omega C + \frac{1}{Rj\omega L}$$


$$\frac{R}{R^2 + (\omega_0 L)^2} - j\omega_0 C - \frac{\omega_0 L}{R^2 + (\omega_0 L)^2}$$

$$\text{Im}[Y(j\omega)]$$


$$C = \frac{L}{R^2 + (\omega_0 L)^2}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \sqrt{1 - \frac{CR^2}{L}}$$

$$1 - \frac{CR^2}{L} > 0$$


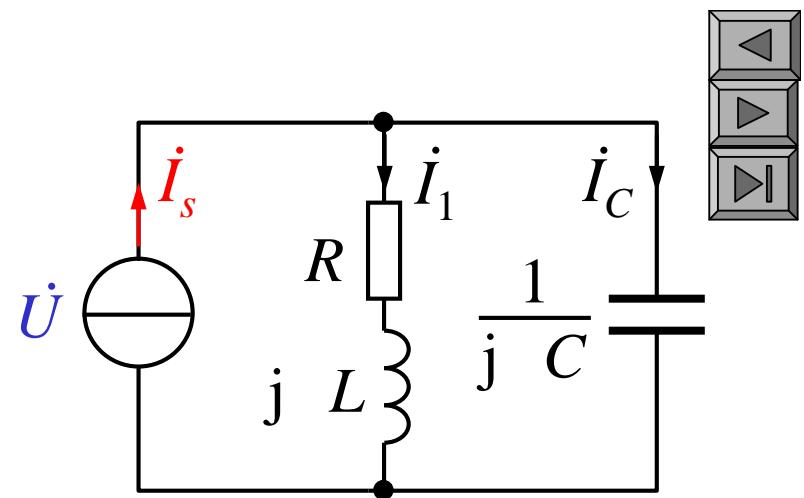

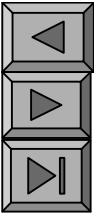
$$\begin{cases} R < \sqrt{\frac{L}{C}} & 0 \\ R > \sqrt{\frac{L}{C}} & \end{cases}$$



$$0 \quad C \quad \frac{L}{R^2} \quad \frac{1}{(L_0)^2}$$
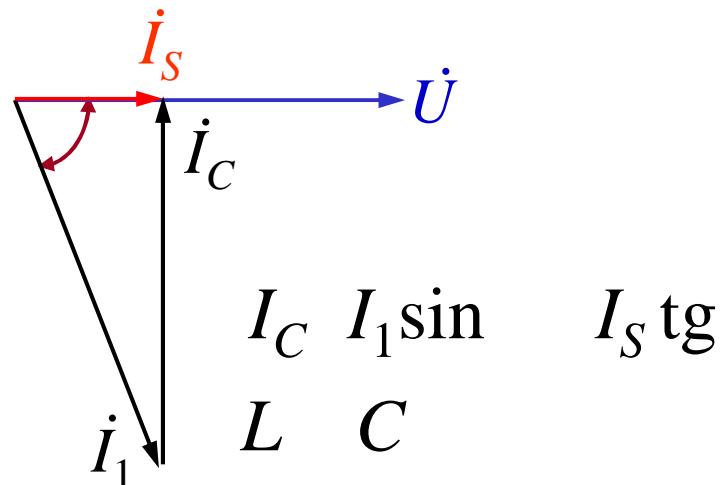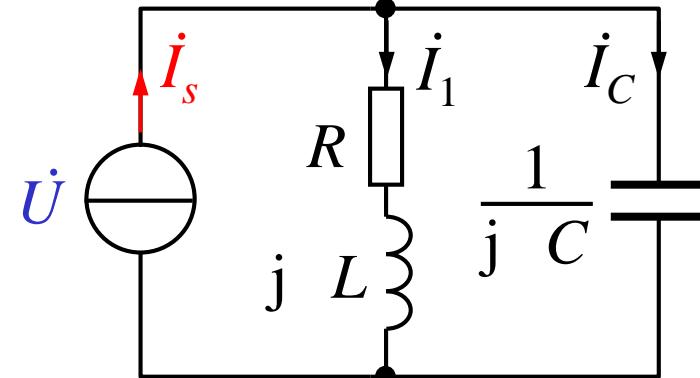
$$Y(j\omega_0) \quad \frac{RC}{L} \quad Z(j\omega_0) \quad \frac{L}{RC}$$



$$0 \quad \frac{1}{\sqrt{LC}} \quad Q \quad \frac{\omega_0 L}{R} \quad \frac{1}{\omega_0 C R}$$

$$\frac{1}{R} \sqrt{\frac{L}{C}} \quad \frac{I_1}{I_s} \quad \frac{I_C}{I_s}$$


Q


$$f = \frac{1}{2\sqrt{LC}}$$

LC

L

C

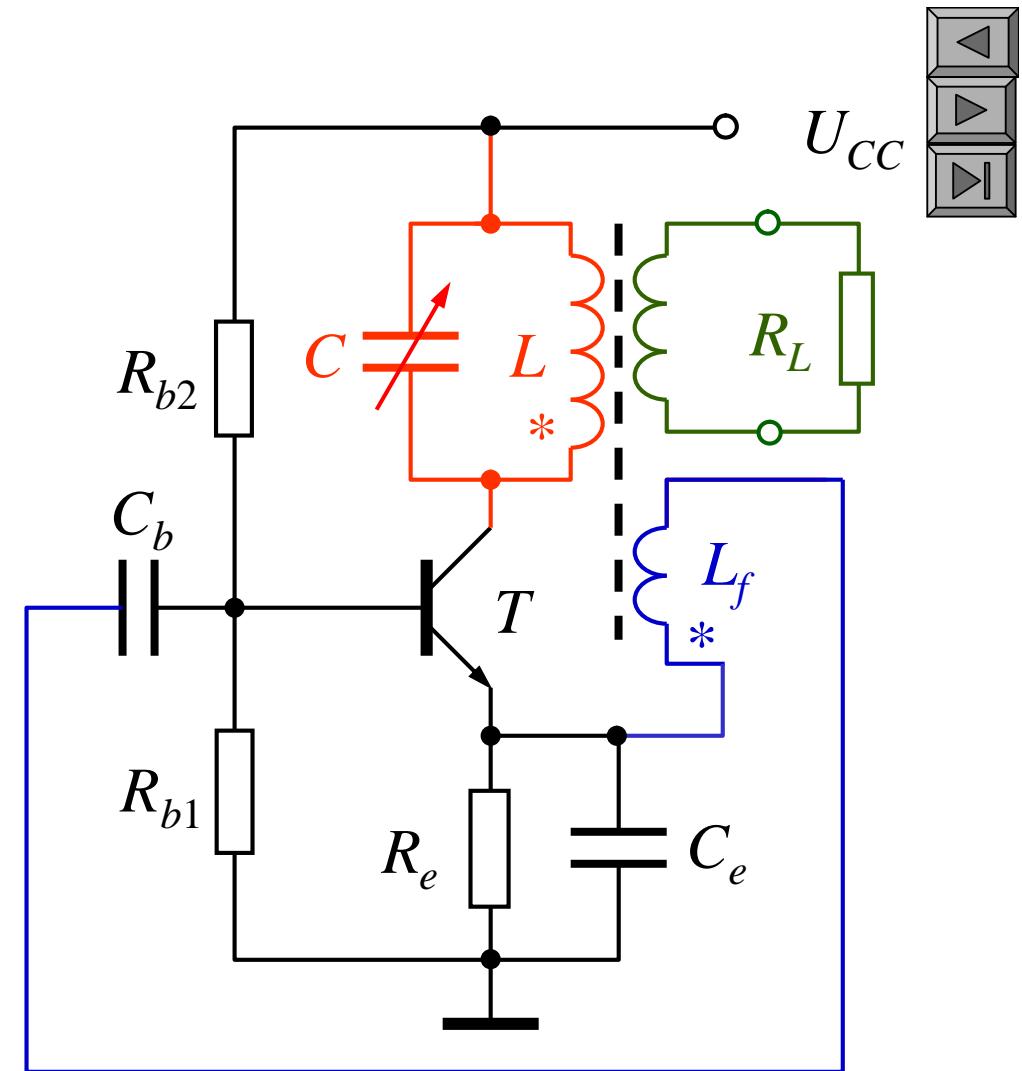


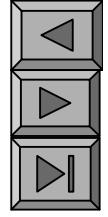

11 5 (Bode)


💡 Bode



lg

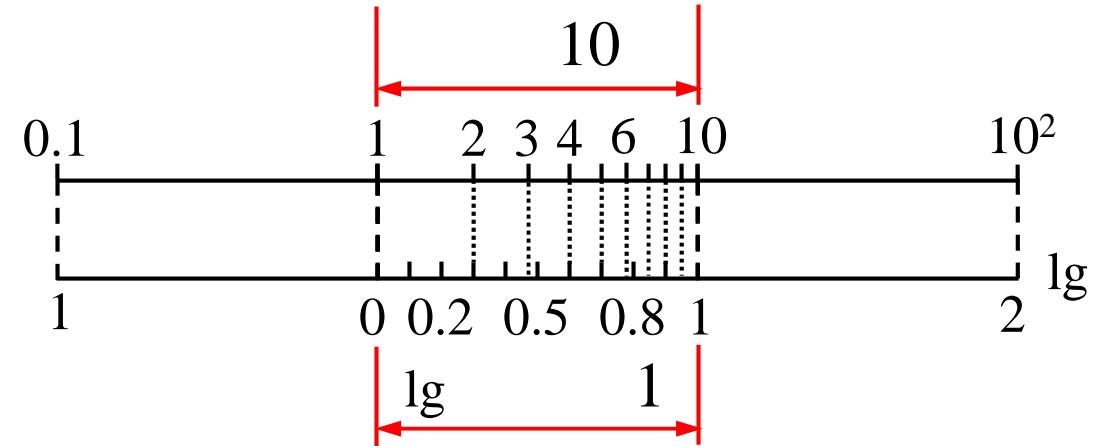


dec
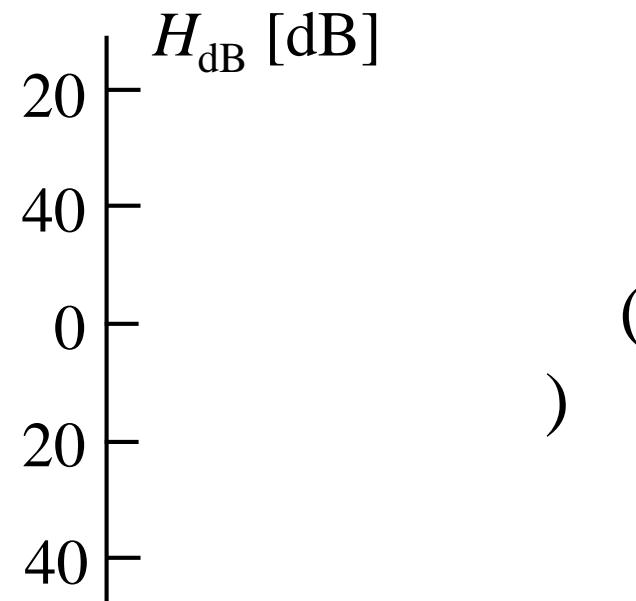
$$H_{\text{dB}} = 20 \lg H(j\omega) \quad (\text{dB})$$



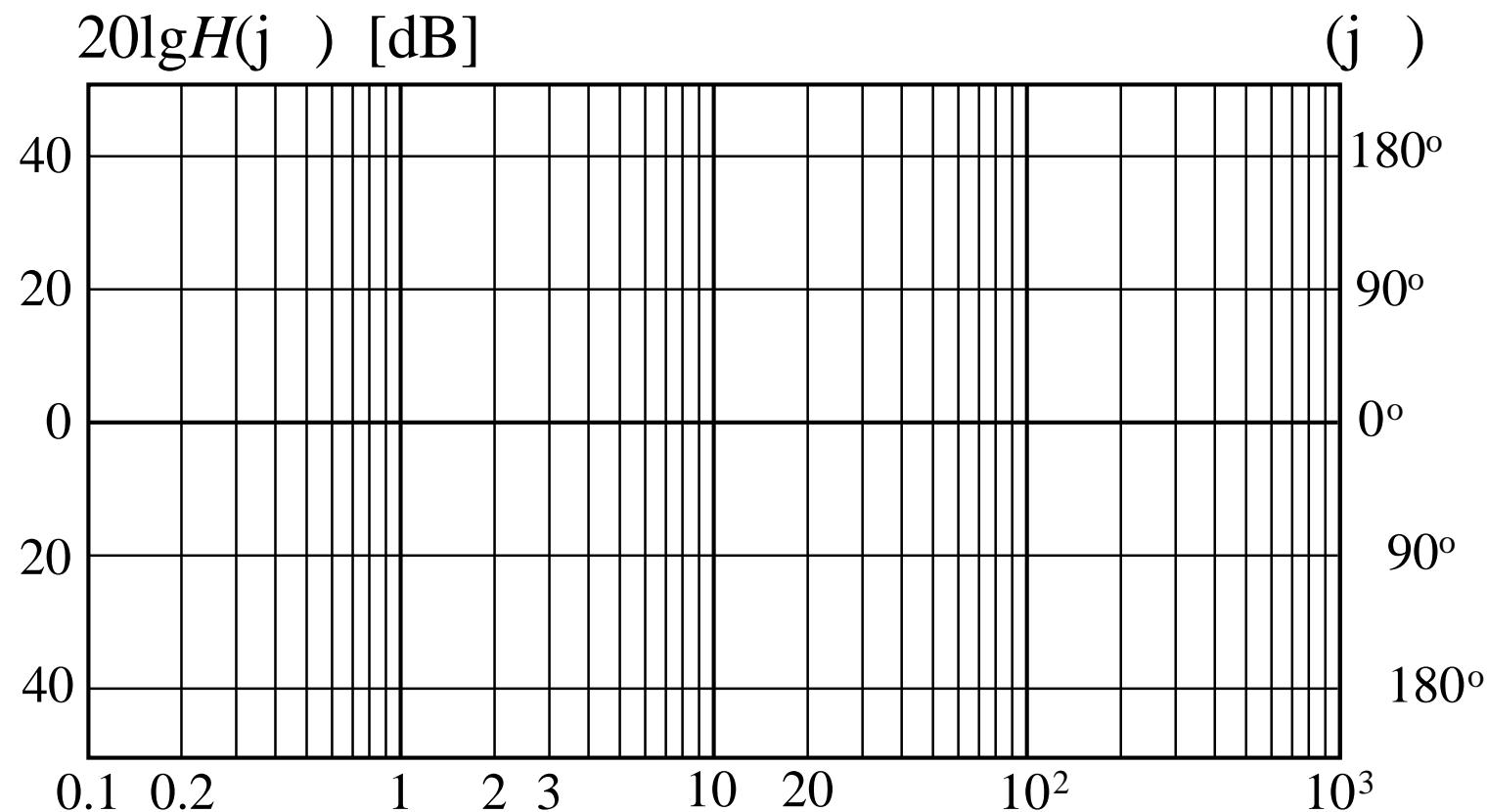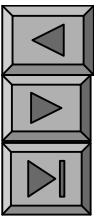

()

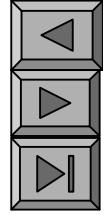

11 4

Bode

$$H(j\omega) = \frac{j200}{(j\omega - 2)(j\omega - 10)} \\ \frac{j10}{(1 - j\omega/2)(1 - j\omega/10)}$$

$$H_{\text{dB}} = 20\lg(10\omega) + 20\lg|1 - j\omega/2| + 20\lg|1 - j\omega/10|$$

$$= 90^\circ \arctg(\omega/2) + \arctg(\omega/10)$$


$$20\lg(10\omega)$$

$$20\lg(10\omega) = 0 \text{ dB}$$


$$20\lg(10\omega) = 0 \text{ dB}$$

$$(0)$$

$$20 \text{ dB / dec}$$

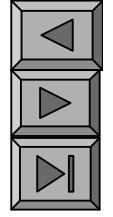

$$\begin{aligned} H_{\text{dB}} &= 20 \lg(10) + 20 \lg|1 + j \cdot 2| + 20 \lg|1 + j \cdot 10| \\ &\quad + 20 \lg|1 + j \cdot 2| \cdot 0d \\ &\quad + 20 \lg|1 + j \cdot 2| - 20 \lg(1/2) \\ &\quad + 20 \lg(1/2) \cdot 0 \quad + 20 \lg(1/2) \quad 20 \text{dB} \\ &\quad + (2 \cdot 0) \quad + 20 \text{dB/dec} \\ 20 \lg|1 + j \cdot 10| &= 20 \lg|1 + j \cdot 10| \cdot 0d \\ &\quad + (10 \cdot 0) \quad + 20 \text{dB/dec} \end{aligned}$$

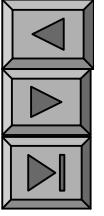

$90^\circ \arctg(\ /2) \arctg(\ /10)$

90°

0.1


0°

10

90°

(0.1~10)


$45^\circ/\text{dec}$

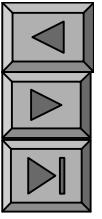




11 6

RC



LC

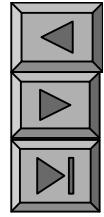



$L \quad C$

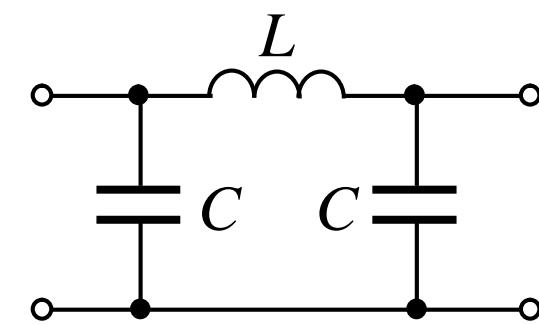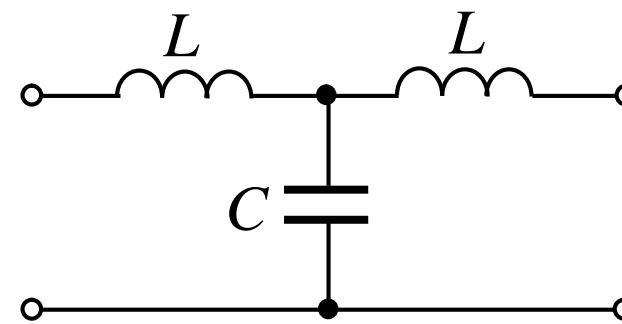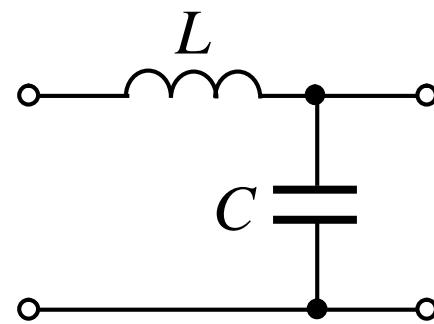

T

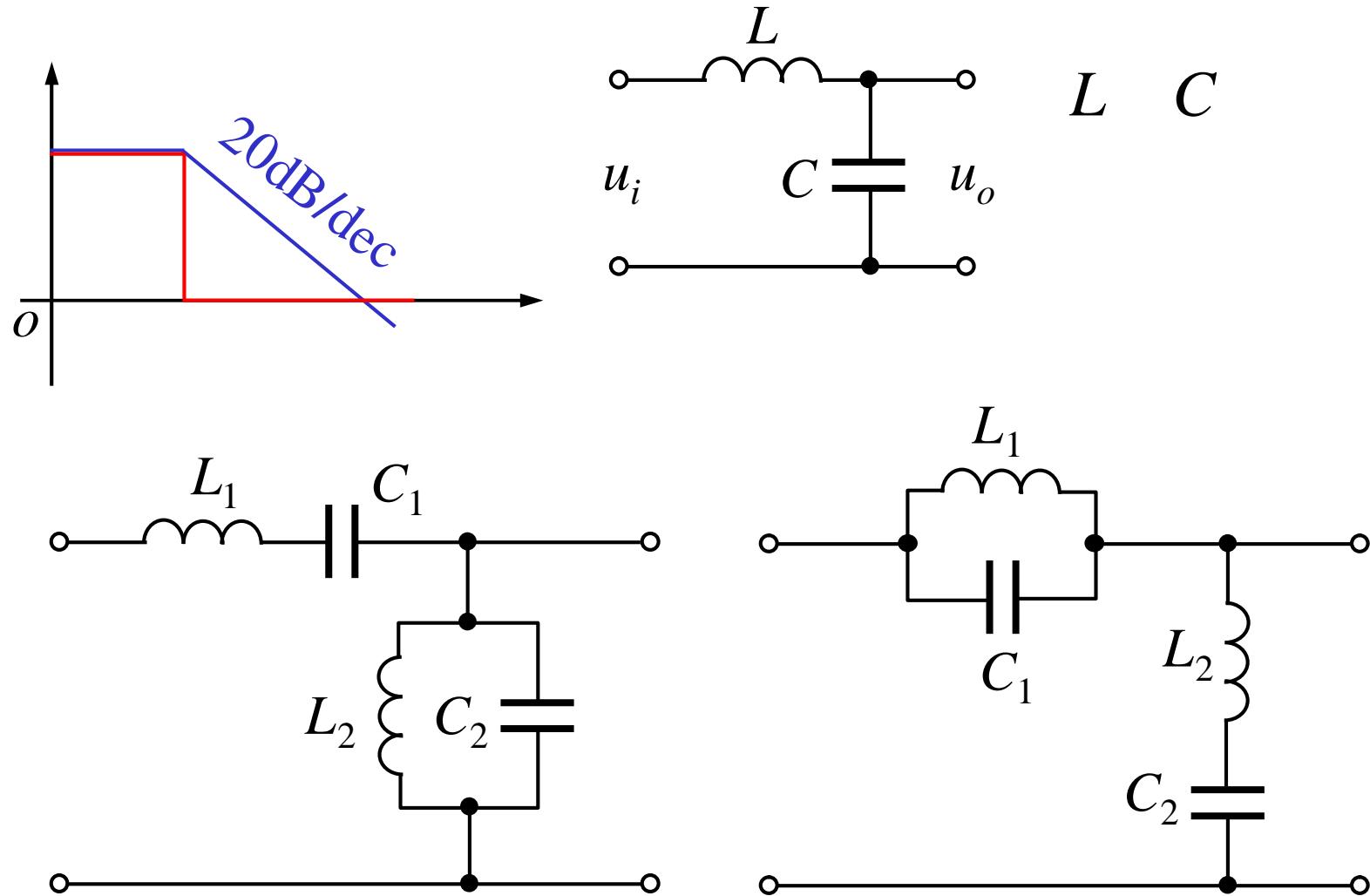
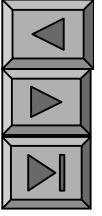


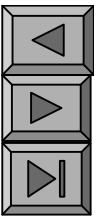


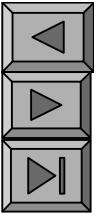

(j)



$20\lg H(j)$ [dB]

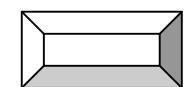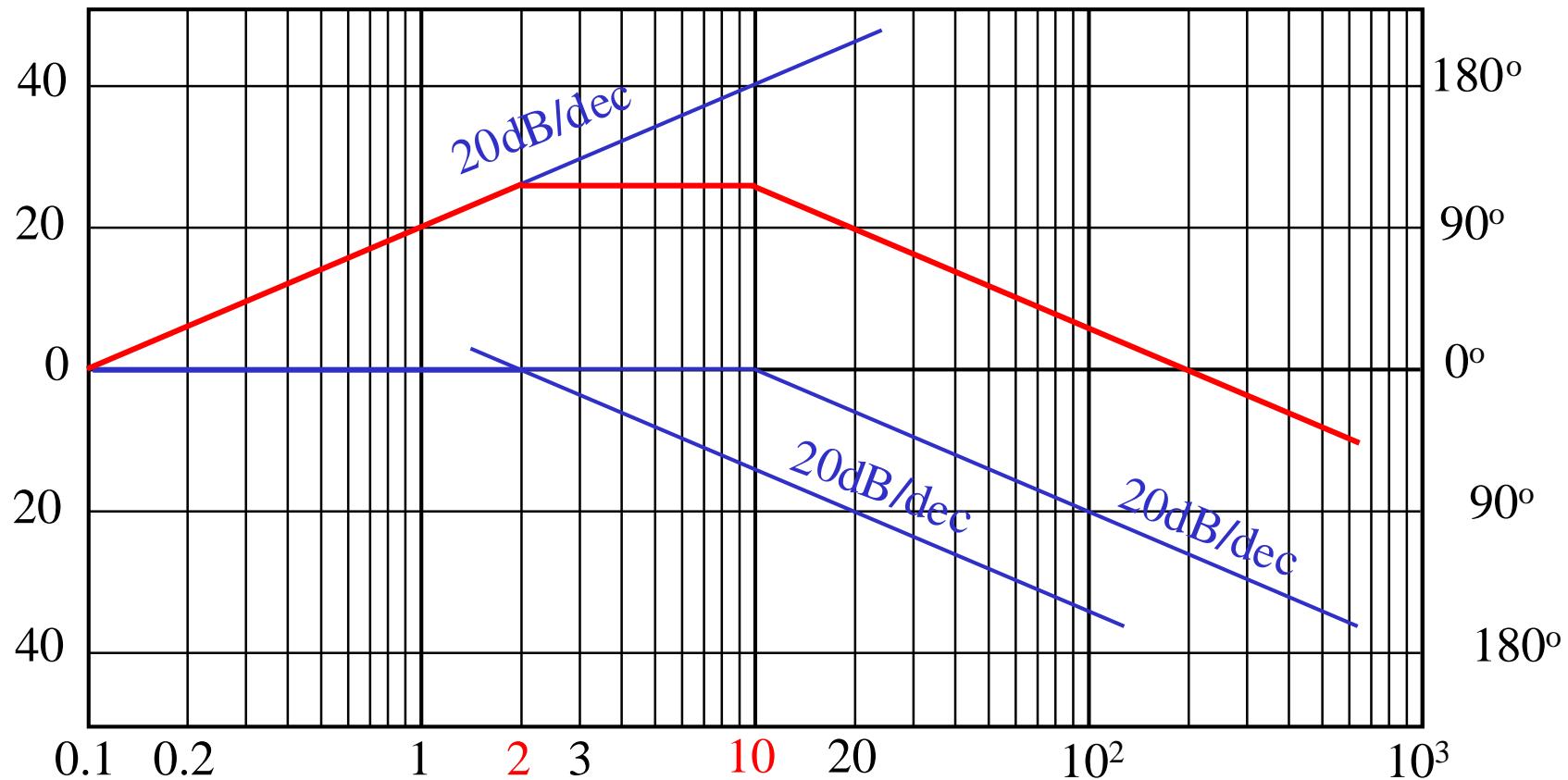


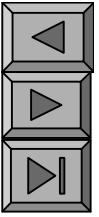

(j)

$20\lg H(j)$ [dB]

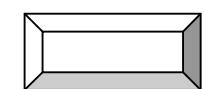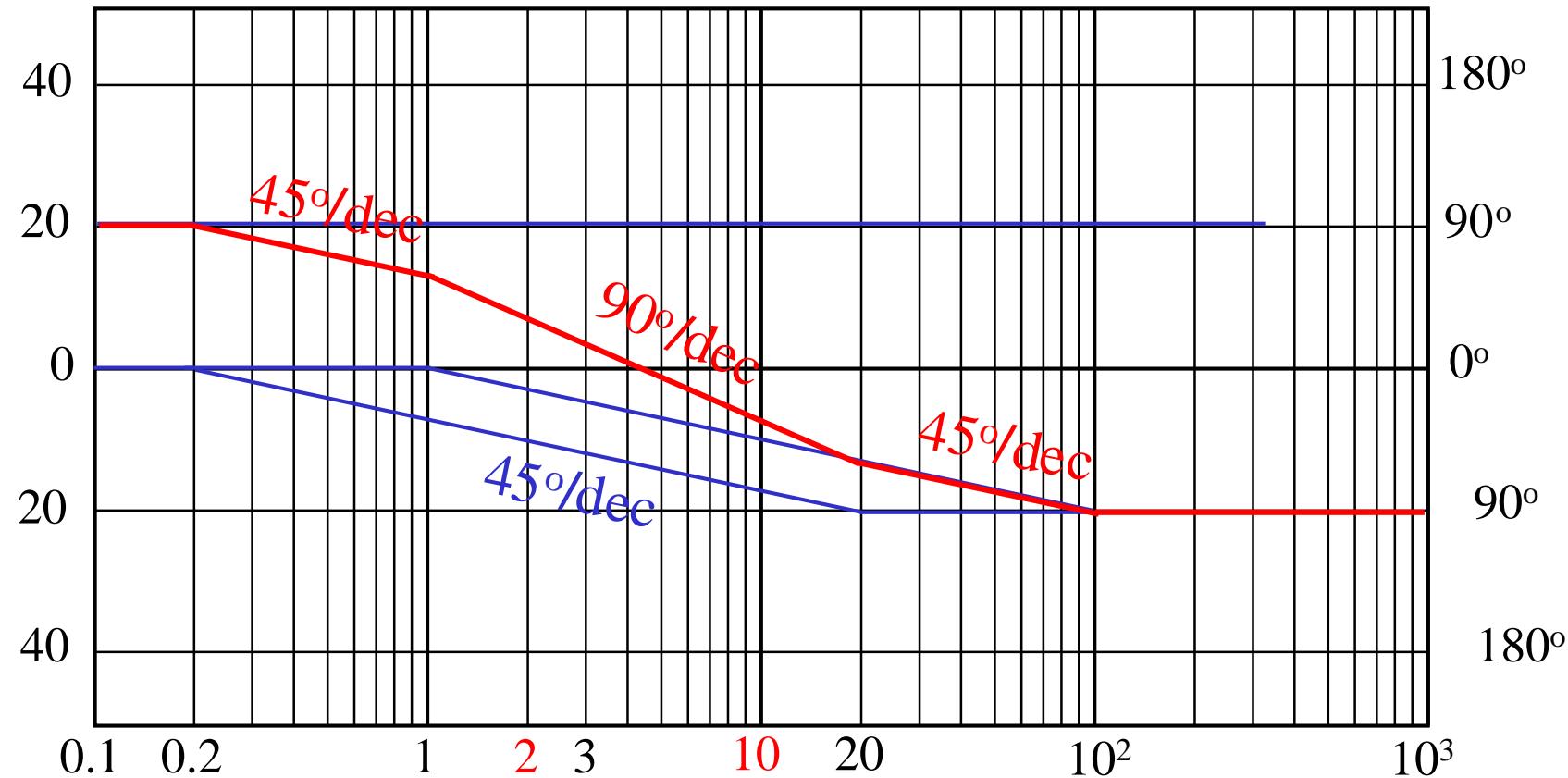

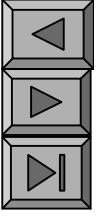

$$11 \quad 19 \quad (1) \quad H(j) \quad \frac{1}{10j}$$

$$H(j) \quad \frac{0.1}{1j}$$

10

$$H_{\text{dB}} = 20\lg 0.1 - 20\lg|1/j|/10$$

10

20dB

$$H_{\text{dB}} = 20\lg 0.1 - 20\lg(/10)$$

(10 20)


20dB/dec

20dB


10


20dB/dec

$$\arctg(/10)$$

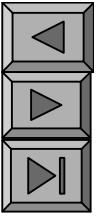
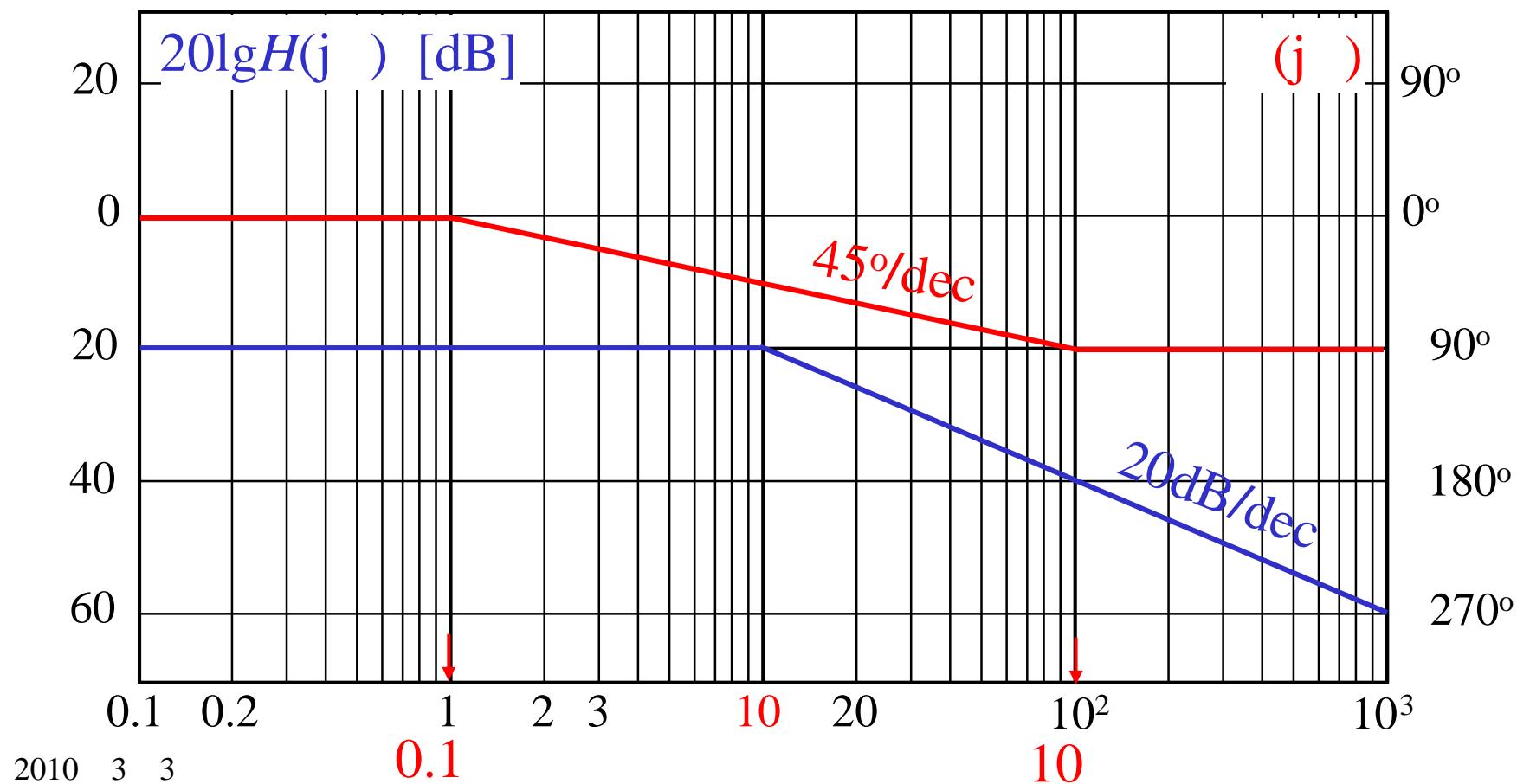
$$\begin{matrix} & 0.1 & (& 10) & 0^\circ \\ 10 & & 90^\circ & (&) \\ (0.1 \sim 10) & & & 45^\circ/\text{dec} & \end{matrix}$$



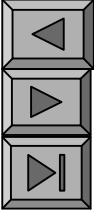

$$11 \quad 19 \quad (2) \quad H(j) \quad \frac{5}{j} \frac{j}{j} \frac{2}{10} \quad \frac{1}{j} \frac{j}{1} \frac{j}{j}$$


$$H_{\text{dB}} = 20 \lg |1/j|/2| + 20 \lg |1/j|/10|$$

$$\begin{aligned} & 20 \lg && (1 \quad 0) \\ & 20 \text{dB/dec} && \end{aligned}$$

+20dB/dec

20dB/dec



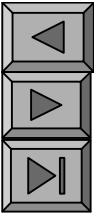

$$H_{\text{dB}} = 20 \lg |1 + j \frac{1}{2}| + 20 \lg |1 + j \frac{1}{10}|$$

$$= 90^\circ + \arctg\left(\frac{1}{2}\right) + \arctg\left(\frac{1}{10}\right)$$

